
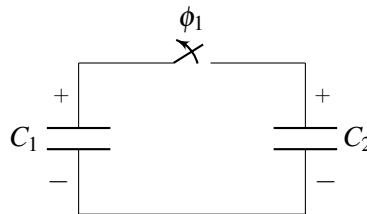


### 1. Capacitors and Charge Sharing

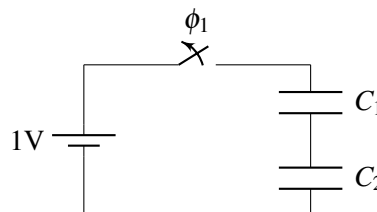- (a) Consider the circuit below, with  $C_1 = C_2 = 1\mu F$ . Suppose initially  $C_1$  is charged to  $+1V$ , and  $C_2$  is charged to  $+2V$ . How much charge is on  $C_1$  and  $C_2$ ? How much energy is stored in each of the capacitors? What is the total stored energy?




- (b) Now the switch is closed (i.e. the capacitors are connected together.) What are the voltages and charges on  $C_1$  and  $C_2$ ? What is the total stored energy?
- (c) Is this more or less energy than before the switch was closed? Why?
- (d) Consider the following circuit, with  $C_1 = 1\mu F$ ,  $C_2 = 3\mu F$ . Suppose both capacitors are initially uncharged ( $0V$ ).



What are the voltages across the capacitors after the switch is closed? What are the charges on the capacitors?

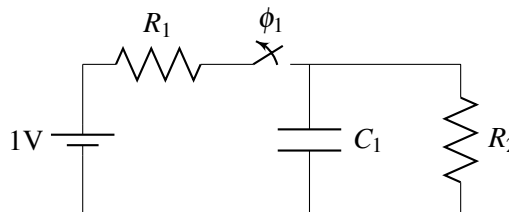
- (e) Consider the circuit below, with  $C_1 = 1\mu F$ ,  $R_1 = 1k\Omega$ ,  $R_2 = 1k\Omega$ .



After the switch is closed, and the circuit is allowed to settle, what is voltage across and current through all circuit elements?

### 2. More Charge Sharing

Consider the following circuit:

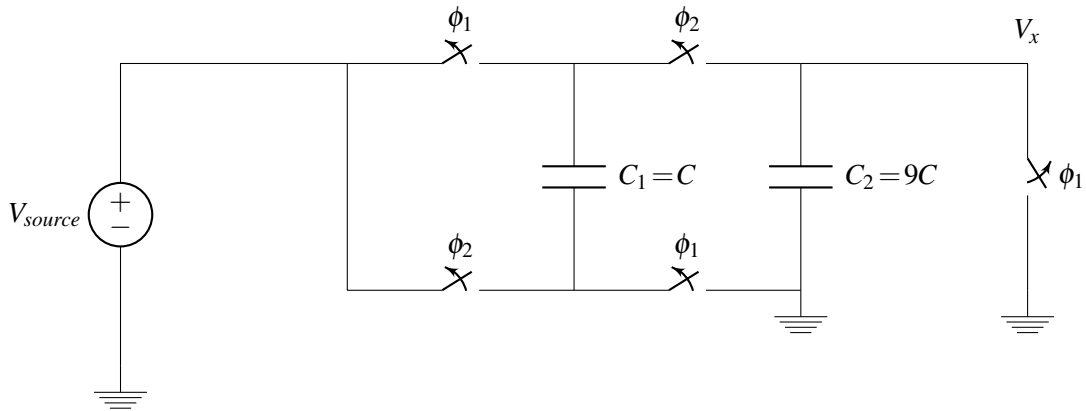

In the first phase, all of the switches labeled  $\phi_1$  will be closed and all switches labeled  $\phi_2$  will be open. In the second phase, all switches labeled  $\phi_1$  open and all switches labeled  $\phi_2$  close.

- Draw polarity of voltage (+ and - signs) on the two capacitors  $C_1$  and  $C_2$ . (It doesn't matter which terminal you label + or -; just remember to keep these consistent through phases 1 and 2!)
- Draw the circuit in the first phase and in the second phase. Keep your polarity in part (a) in mind.
- Find the voltages and charges on  $C_1$  and  $C_2$  in the first phase. Be sure to keep the polarities of the voltages the same!
- Now, in the second phase, find the voltage  $V_x$ .
- (BONUS) If capacitor  $C_2$  did not exist (i.e., had a capacitance of 0F), what would the voltage  $V_x$  be?